

# Sithney C.P. School Knowledge Organisers



## Science. Physics: Electricity

### What you should already know:

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.

### Key learning:

- Adding more cells to a complete circuit will make a bulb brighter, a motor spin faster or a buzzer make a louder sound.
- If you use a battery with a higher voltage, the same thing happens.
- Adding more bulbs to a circuit will make each bulb less bright.
- Using more motors or buzzers, each motor will spin more slowly and each buzzer will be quieter.
- Turning a switch off (open) breaks a circuit so the circuit is not complete and electricity cannot flow. Any bulbs, motors or buzzers will then turn off as well.
- You can use recognised circuit symbols to draw simple circuit diagrams.

### Key Vocabulary:

**Battery/cell:** A stored source of electricity.

**Bulb/lamp:** A glass bulb which provides light by passing an electrical current through a filament.

**Buzzer:** An electrical device that makes a buzzing noise and is used for signalling (for example, in a burglar alarm).

**Circuit diagram:** see example provided.

**Complete circuit:** A complete and closed path around which a circulating current can flow.

**Conductor:** an object that allows electricity to flow through it easily (objects made of metal are good conductors).

**Current:** A flow of electricity which results from the ordered directional movement of electrically charged particles.

**Electricity:** A form of energy caused by electrons moving.


**Insulator:** An object that does not allow electricity to flow through it easily.

**Motor:** A machine that turns electrical energy into Movement.


**Switch:** A switch turns an electrical circuit on or off by completing or breaking the circuit.

**Voltage:** The force that makes electricity move through a wire.

## Circuit Diagram Symbols

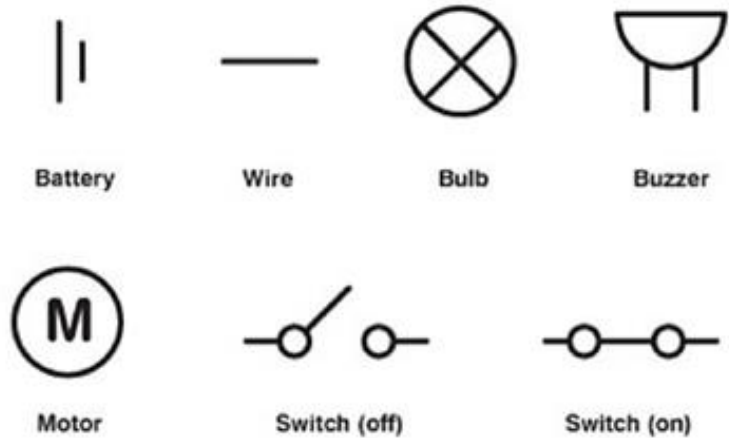

## Circuit Diagram

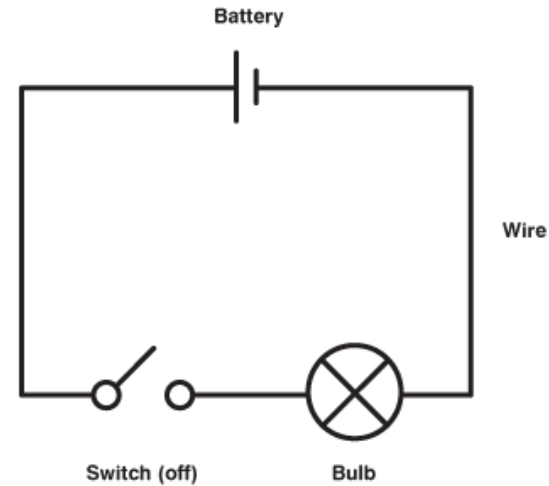

## Scientific Method: planning an investigation

### Variables

Choose your **independent variable** (what you will change) and your **dependent variable** (what you will measure)

### Question

Create your question: what is the effect of changing the (**independent variable**) on the (**dependent variable**).

### Prediction

Make a prediction of what you think will happen based on what you already know.

### Equipment

List all of the equipment you will use.

### Method

Describe the method using numbered bullet points.

### Risks

Identify any risks you must be aware of to ensure safety.